

# Tutor Marked Assignment #1 | 2021

- Submit your written assignment to the drop box provided in the Moodle on or before **11<sup>th</sup> July 2022**; late submissions will not be accepted!
- Clearly show your assumptions, if any, when you answer the questions.

**[Q1]** Consider the following Boolean functions F1, F2, F3 and F4.

3,5,9,7

$$F1(w, x, y, z) = \Sigma(0, 1, 5),$$

$$F2(w, x, y, z) = \Pi(a, b, c, d)$$

$$F3(w, x, y, z) = \Sigma(2, 6, 10, 12, 14, 15),$$

$$F4(w, x, y, z) = \Sigma(a, b, c, d)$$

Where  $a, b, c$ , and  $d$ , are the last four digits of your registration number.

- Draw the K-map for F1, F2, F3, F4 and find optimize expressions for F1, F2, F3, F4.
- Draw truth tables for the above expressions.
- Draw circuit diagrams to realize the same functions by using the following PLDs. (Clearly, show the size of the each PLD)
  - ROM
  - PLA
  - PAL
- Compare and contrast each implementation above.

**[Q2]**

- Draw a timing diagram and show how the propagation delay affects the T-Flip Flop using an example. (Clearly, show the propagation delay, setup time, hold time, and clock period of your example).
- Hence derive the equations showing the relations between propagation delay, setup time, hold time, and clock period.
- Figure 1 depicts a network which has inputs ( $X, T_A$ ) and output ( $Q_A, Q'_A$ ) as below. Where; HIGH to LOW propagation delay ( $t_{PHL}$ ) = 100 ns, LOW to HIGH propagation delay ( $t_{PLH}$ ) = 60 ns, set-up time ( $t_{SU}$ ) = 20 ns, hold time ( $t_H$ ) = 0 ns, maximum clock frequency ( $f_{CLKMAX}$ ) = 10MHz.

Draw a timing diagram for the network showing  $X, T_A, Q'_A$ . Assume that  $X$  is initially 1 and  $X$  becomes 0 for 10 ns, then  $X$  becomes 1 for 180 ns. Clearly, state other assumptions, if any.

 


Figure 1

**[Q3]**

- Draw a block diagram of the 1-bit Full Adder (FA).
- Implement the data flow model of the 1-bit FA using the VHDL program.
- Write the Test Bench model for the 1-bit FA.

### [Q4]

- (a) Draw a block diagram of the 4-bit FA using 1-bit FAs.
- (b) Implement the data flow model of the 4-bit FA using the VHDL program.
- (c) Write the Test Bench model for the 4-bit FA.

### [Q5]

- (a) Briefly explain the method of integrating propagation delay into your VHDL simulation.
- (b) Modify the Test bench written in Q5.c with suitable delays.
- (c) Modify the same test bench written in Q5.c with a file I/O. You may use text files to read inputs and write output signals.